

EE2703: ASSIGNMENT 7

KORRA SRIKANTH

EE19B033

May 14, 2021

1 Introduction

The aim of this assignment is to analyse circuits using the Symbolic algebra capabilities of `Sympy`.

Low-Pass Filter

In this section, we analyse the low pass filter circuit of output:

$$V_o(s) = \frac{-0.0001586 \cdot V_i(s)}{2 \times 10^{-14}s^2 + 4.414 \times 10^{-9}s + 0.0002} \quad (1)$$

From (1), we get the step response of the circuit as:

$$V_o(s) = \frac{-0.0001586 \cdot \frac{1}{s}}{2 \times 10^{-14}s^2 + 4.414 \times 10^{-9}s + 0.0002} \quad (2)$$

Now, we can easily create a `signal.lti` object with the coefficients we got, and use `signal.bode` to obtain the magnitude plot, which is shown below.

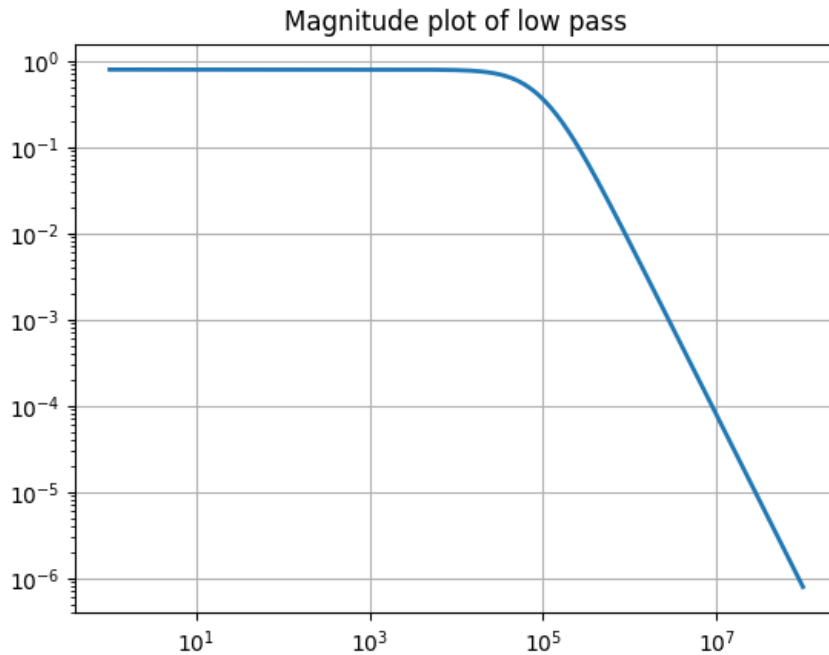


Figure 1: Bode Magnitude of LPF

To see the step response of the system, we can use `signal.step`. The step response of the system is shown below.

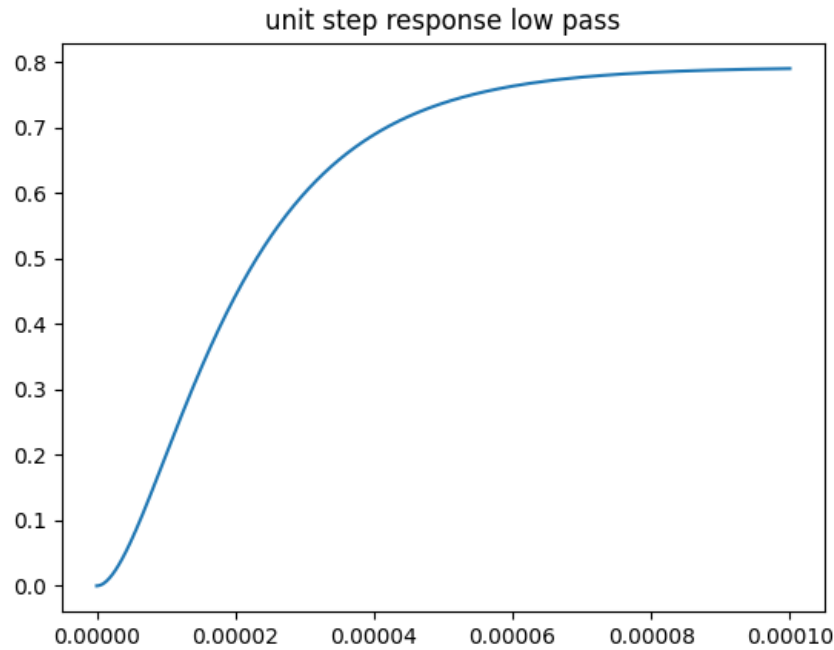


Figure 2: Step response of LPF

2 High-Pass Filter

We shall now look at a slightly modified version of the above circuit.

Code:

```
#highpass Function
def highpass(R1,R2,C1,C2,G,Vi):
    s=sy.symbols('s')
    A=sy.Matrix([[0,0,1,-1/G],[-(s*R2*C2)/(1+s*R2*C2),1,0,0],[0,-G,G,1],[-1/R1-s*C2-s*C1,s*C2]])
    b=sy.Matrix([0,0,0,-Vi*s*C1])
    V = A.inv()*b
    return (A,b,V)

#Highpass Filter
A,b,V=highpass(10000,10000,1e-9,1e-9,1.586,1)
Vo=V[3]
w=np.logspace(0,8,801)
ss=1j*w
s = sy.symbols('s')
hf=sy.lambdify(s,Vo,'numpy')
v=hf(ss)
plt.loglog(w,abs(v),lw=2)
plt.title(r'Magnitude plot of High pass')
plt.grid(True)
plt.show()
```

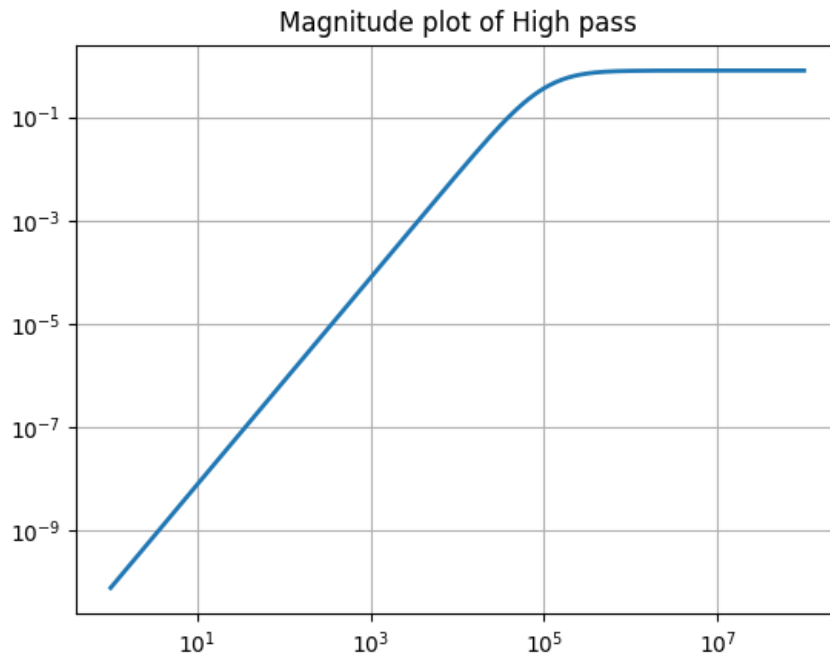


Figure 3: Bode Magnitude plot of HPF

Computing the Sinusoidal Response of Highpass Filter

Code:

```
Vo_signal = convert(Vo)
# computes the sinusoidal response of the highpass
t = \np.linspace(0,6/(1e6),2001)
Si = np.sin(2000*np.pi*t)+np.cos(2*1e6*np.pi*t)
t,sin_res,svec = sp.lsim(Vo_signal,Si,t)

fig, axes = plt.subplots(1, 2, \figsize=(12, 5), sharey = True)
axes[0].plot(t,sin_res)
axes[0].grid()
axes[0].set_title(' Output of highpass filter to given sinusoidal Input  ')
axes[0].set_xlabel('Time')
axes[0].set_ylabel('y(t)')

axes[1].plot(t,Si)
axes[1].grid()
axes[1].set_title(' Input to highpass filter')
axes[1].set_xlabel('Time')
axes[1].set_ylabel('x(t)')
plt.show()
```

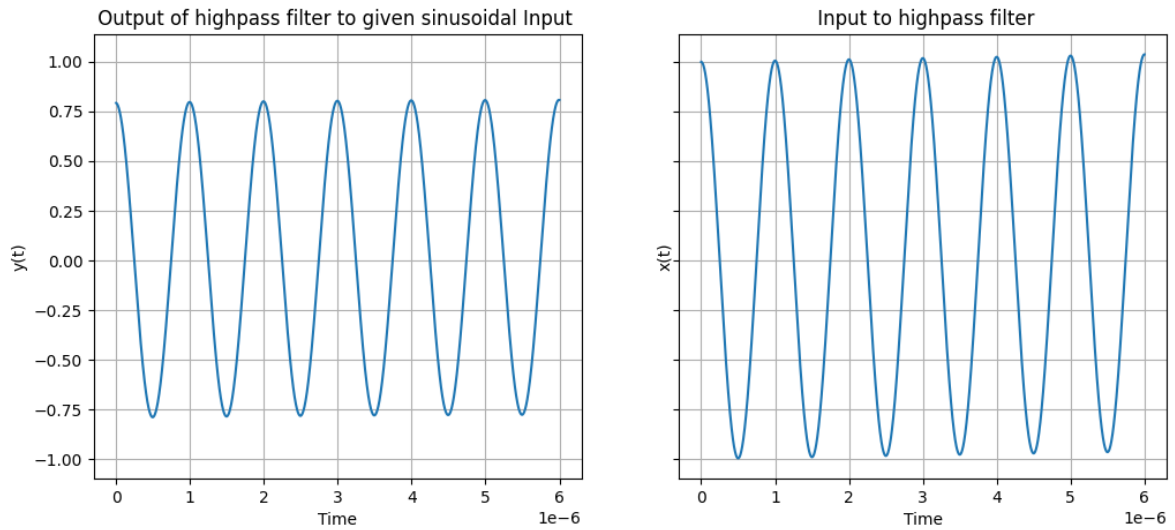


Figure 4: Sinusoidal Response of Highpass Filter

Computing the Damped Sinusoidal Response of Highpass Filter

Code:

```
t = np.linspace(0.0,3e-5,100001)
Di = np.exp(-1e5*t)*np.cos(2*1e6*np.pi*t)
t,sin_res,svec = sp.lsim(Vo_signal,Di,t)

fig, axes = plt.subplots(1, 2, figsize=(12, 5), sharey = True)
axes[0].plot(t,sin_res)
axes[0].grid()
axes[0].set_title('Output of highpass filter to given damping input')
axes[0].set_xlabel('Time')
axes[0].set_ylabel('y(t)')
axes[1].plot(t,Di)
axes[1].grid()
axes[1].set_title('Input to highpass filter')
axes[1].set_xlabel('Time')
axes[1].set_ylabel('x(t)')
plt.show()
```

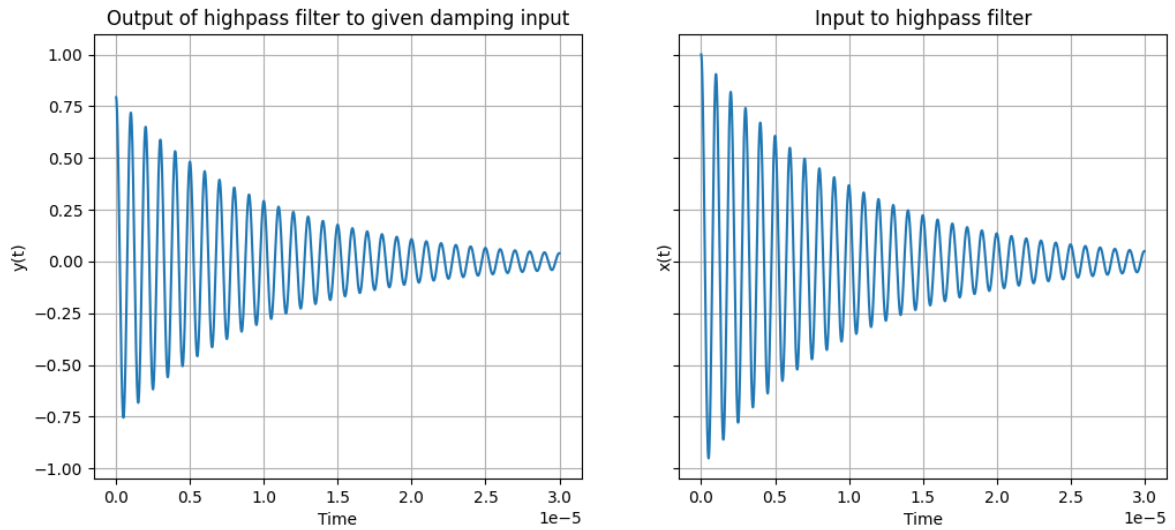


Figure 5: Damped Sinusoidal Response of Highpass Filter

Computing the Step Response of input(1/s)

Code:

```
# The below code computes the unit step response by passing the Vi as 1/s
A,b,V=lowpass(10000,10000,1e-9,1e-9,1.586,1/s)
Vo=V[3]
Vo_signal = convert(Vo)
t,Vo_time = sp.impulse(Vo_signal,None,np.linspace(0,100e-6,20001))
plt.plot(t,Vo_time)
plt.grid()
plt.title('step response of lowpass(1/s)')
plt.plot()
plt.show()

A,b,V=highpass(10000,10000,1e-9,1e-9,1.586,1/s)
Vo=V[3]
Vo_signal = convert(Vo)
t,Vo_time = sp.impulse(Vo_signal,None,np.linspace(0,100e-6,20001))
plt.plot(t,Vo_time)
plt.grid()
plt.title('step response of Highpass(1/s)')
plt.plot()
plt.show()
```

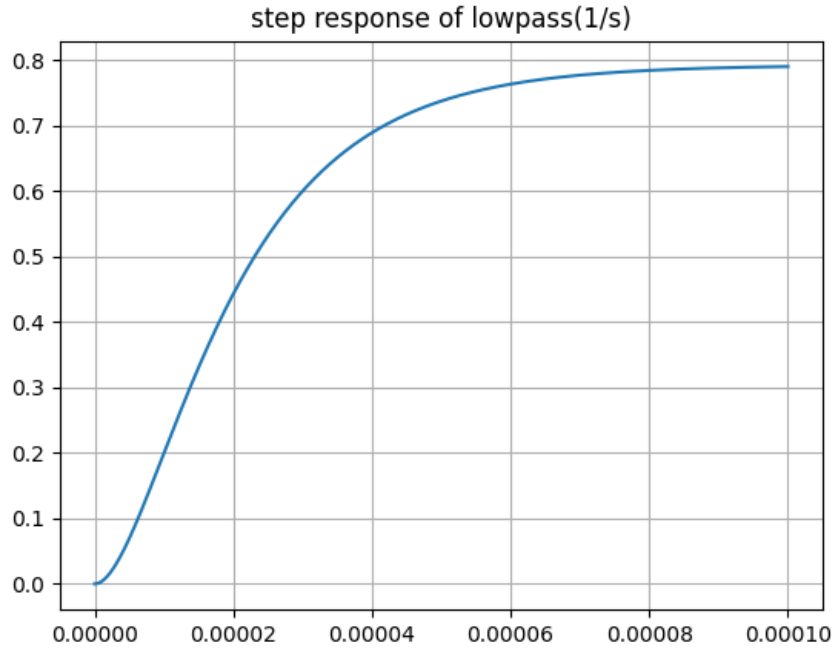


Figure 6: Step Response of LPF

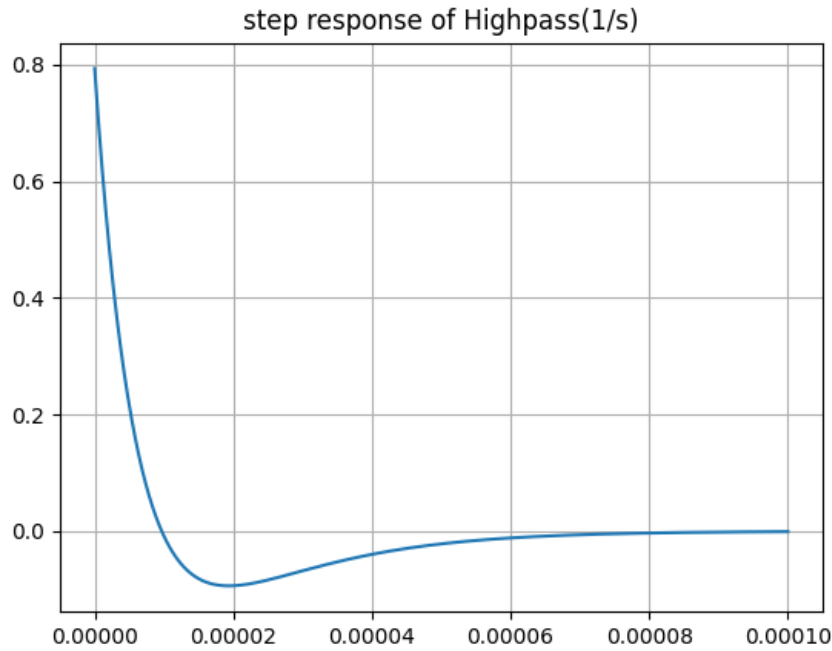


Figure 7: Step Response of HPF

3 Conclusion

Sympy provides a convenient way to analyse LTI systems using their Laplace transforms. The toolbox was used to study the behaviour of a low pass filter, implemented using an op-amp of gain G . For a mixed frequency sinusoid as input, it was found that the filter suppressed the high frequencies while allowing the low frequency components. Similarly, a high pass filter was implemented using an op-amp with the same gain. The magnitude response of the filter was plotted and its output was analysed for damped sinusoids. The step response of the filter was found to have a non-zero peak at $t = 0$, due to the sudden change in the input voltage.